



西安交通大学  
XI'AN JIAOTONG UNIVERSITY



人工智能学院  
College of Artificial Intelligence, XJTU

# 数字设计和计算机体系结构


## 第四章 硬件描述语言HDL

刘龙军 副教授

2020年11月7日
 
# 第四章 硬件描述语言

- 介绍
- 组合逻辑
- 结构化模块
- 时序逻辑
- 更多组合逻辑
- 有限状态机
- 参数化模块
- 测试程序



# 介绍

- Hardware description language (HDL):
  - specifies logic function only
  - Computer-aided design (CAD) tool produces or *synthesizes* the optimized gates
- Most commercial designs built using HDLs
- Two leading HDLs:
  - **SystemVerilog**
    - developed in 1984 by Gateway Design Automation
    - IEEE standard (1364) in 1995
    - Extended in 2005 (IEEE STD 1800-2009)
  - **VHDL 2008**
    - Developed in 1981 by the Department of Defense
    - IEEE standard (1076) in 1987
    - Updated in 2008 (IEEE STD 1076-2008)

# HDL to Gates

- 仿真

- Inputs applied to circuit
- Outputs checked for correctness
- Millions of dollars saved by debugging in simulation instead of hardware

- 综合

- Transforms HDL code into a *netlist* describing the hardware (i.e., a list of gates and the wires connecting them)

# HDL to Gates

- 仿真


- Inputs applied to circuit
- Outputs checked for correctness
- Millions of dollars saved by debugging in simulation instead of hardware

- 综合

- Transforms HDL code into a *netlist* describing the hardware (i.e., a list of gates and the wires connecting them)

**IMPORTANT:** When using an HDL, think of the **hardware** the HDL should implies (当使用HDL时, 要时时想到实现的硬件)

# SystemVerilog Modules

 

## Two types of Modules:

- **行为级**: describe what a module does
- **结构**: describe how it is built from simpler modules

# 行为级描述 SystemVerilog

## SystemVerilog:

```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```

# Behavioral SystemVerilog

## SystemVerilog:

```
module example(input  logic a, b, c,
               output logic y);
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;
endmodule
```


- module/endmodule: required to begin/end module
- example: name of the module
- Operators:
  - ~: NOT
  - &: AND
  - |: OR



# HDL 仿真

## SystemVerilog:

```
module example(input logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```

 


# HDL 综合

## SystemVerilog:

```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```

## Synthesis:

 

# SystemVerilog 语法

- 大小写敏感的
  - **Example:** `reset` and `Reset` are not the same signal.
- 命名不能以数字开头
  - **Example:** `2mux` is an invalid name
- 空格被忽略
- 注释:
  - `//` single line comment
  - `/*` multiline  
comment `*/`

# Structural Modeling - 层次化

```
module and3(input  logic a, b, c,  
            output logic y);  
    assign y = a & b & c;  
endmodule
```


```
module inv(input  logic a,  
           output logic y);  
    assign y = ~a;  
endmodule
```

```
module nand3(input  logic a, b, c  
             output logic y);  
    logic n1;                // 内部信号  
    and3 andgate(a, b, c, n1); // 实例: and3  
    inv  inverter(n1, y);     // 实例: inv  
endmodule
```

# 位操作符Operators

```
module gates(input logic [3:0] a, b,  
             output logic [3:0] y1, y2, y3, y4, y5);  
  /* Five different two-input logic  
     gates acting on 4 bit busses */  
  assign y1 = a & b;      // AND  
  assign y2 = a | b;      // OR  
  assign y3 = a ^ b;      // XOR  
  assign y4 = ~(a & b);   // NAND  
  assign y5 = ~(a | b);   // NOR  
endmodule
```

综合后:

 

// single line comment


/\*...\*/ multiline comment

# 位与运算Operators

## SystemVerilog:

```
module and8(input logic [7:0] a,  
           output logic      y);  
    assign y = &a;  
    // &a is much easier to write than  
    // assign y = a[7] & a[6] & a[5] & a[4] &  
    //           a[3] & a[2] & a[1] & a[0];  
endmodule
```

## 综合后:

 


# 条件赋值语句

## SystemVerilog:

```
module mux2(input  logic [3:0] d0, d1,  
            input  logic      s,  
            output logic [3:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```

## 综合后:

 


? : is also called a *ternary operator* because it operates on 3 inputs: s, d1, and d0.

# 内部变量


## SystemVerilog:

```
module fulladder(input  logic a, b, cin,  
                output logic s, cout);  
  
    logic p, g;    // internal nodes  
  
    assign p = a ^ b;  
    assign g = a & b;  
  
    assign s = p ^ cin;  
    assign cout = g | (p & cin);  
endmodule
```

## Synthesis:

 



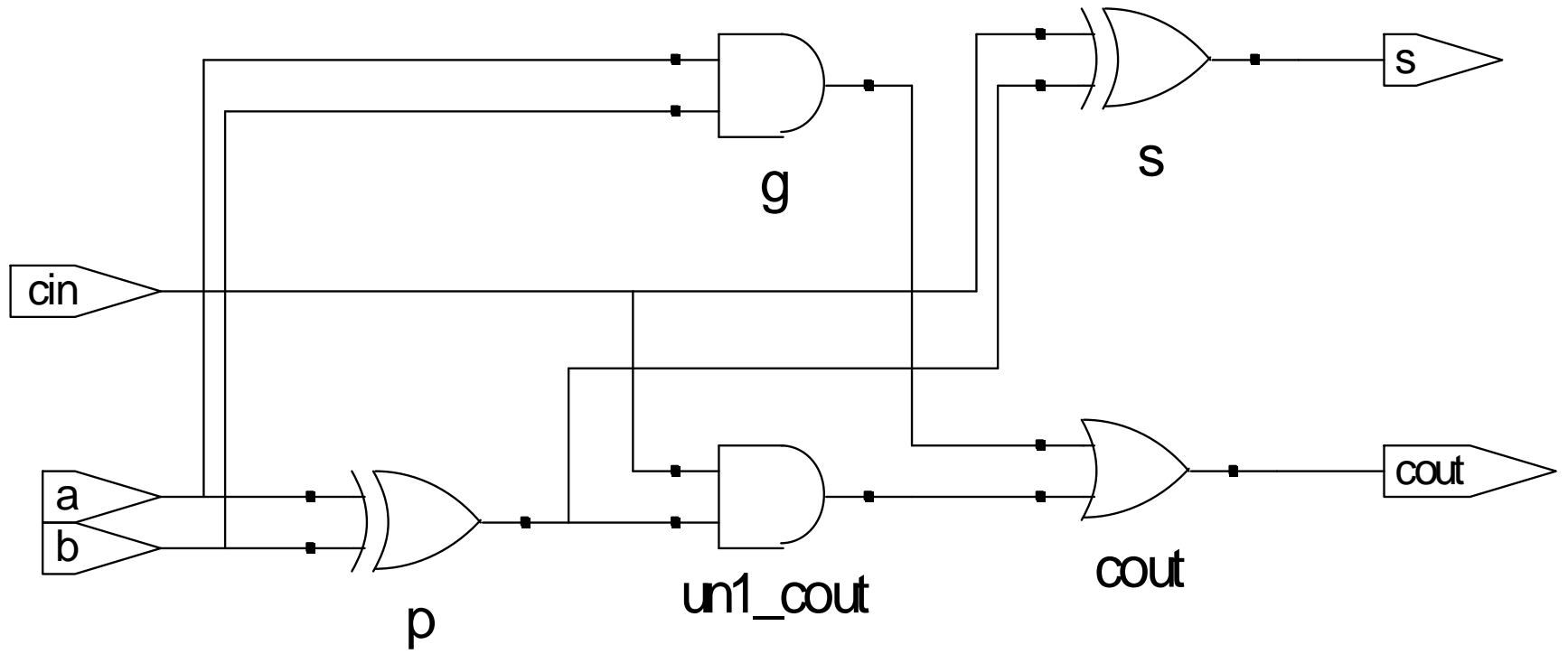

## 测试模块：

```
module test_full_adder;
logic    a, b;
logic    cin;
initial begin
            a = 1'b1; b=1'b1; cin=1'b1;
        #10 a = 1'b0; b=1'b0; cin=1'b0;
        #10 a = 1'b0; b=1'b1; cin=1'b1;
        #10 a = 1'b1; b=1'b0; cin=1'b1;
        #10 $stop; end
full_adder  n1(a, b, cin, s, cout);
endmodule
```

# 优先级










Highest

~	NOT
*, /, %	mult, div, mod
+, -	add, sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=, >, >=	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, NOR
? :	ternary operator

Lowest
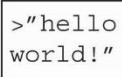
# 第四章 硬件描述语言

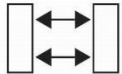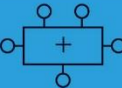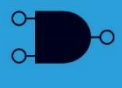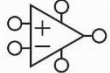- 介绍
- 组合逻辑
- 结构化模块
- 时序逻辑
- 更多组合逻辑
- 有限状态机
- 参数化
- 测试程序

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

# 数制

## Format: N'B value

**N** = number of bits, **B** = base

**N'B** is optional but recommended (default is decimal)

Number	# Bits	Base	Decimal Equivalent	Stored
3'b101	3	binary	5	101
'b11	unsized	binary	3	00...0011
8'b11	8	binary	3	00000011
8'b1010_1011	8	binary	171	10101011
3'd6	3	decimal	6	110
6'o42	6	octal	34	100010
8'hAB	8	hexadecimal	171	10101011
42	Unsized	decimal	42	00...0101010

# 位操作: Example 1

```
assign y = {a[2:1], {3{b[0]}}, a[0], 6'b100_010};
```

```
// if y is a 12-bit signal, the above statement produces:
```

```
y = a[2] a[1] b[0] b[0] b[0] a[0] 1 0 0 0 1 0
```

```
// 下划线 _ are used for formatting only to make
```

```
// it easier to read. SystemVerilog ignores them.
```


# 位操作: Example 2

## SystemVerilog:

```
module mux2_8(input  logic [7:0] d0, d1,
             input  logic      s,
             output logic [7:0] y);

    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);
endmodule
```

## Synthesis:

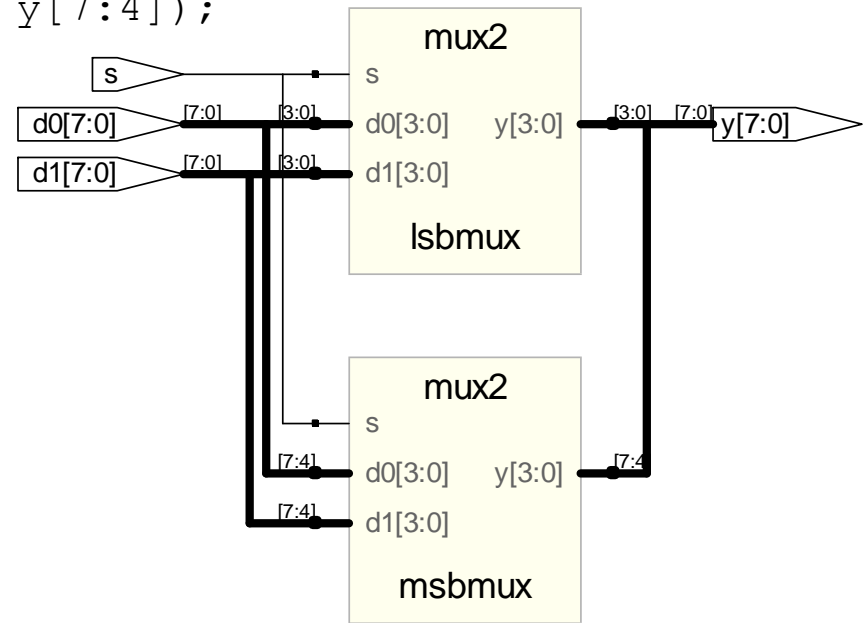


# Z: 高阻输出

## SystemVerilog:

```
module tristate(input  logic [3:0] a,  
               input  logic      en,  
               output tri  [3:0] y);  
    assign y = en ? a : 4'bz;  
endmodule
```

## Synthesis:

 




# 延迟设置

```
module example(input logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} = ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

```
module test_example;  
    reg a,b,c;  
    initial begin  
        a = 1'b0; b=1'b0; c=1'b0;  
        #10 a = 1'b0; b=1'b0; c=1'b1;  
        #10 a = 1'b0; b=1'b1; c=1'b0;  
        #10 a = 1'b0; b=1'b1; c=1'b1;  
        #10 a = 1'b1; b=1'b0; c=1'b0;  
        #10 a = 1'b1; b=1'b0; c=1'b1;  
        #10 a = 1'b1; b=1'b1; c=1'b0;  
        #10 a = 1'b1; b=1'b1; c=1'b1;  
        #10 $stop;  
    end  
    example example_instance(a, b, c, y);  
endmodule
```

# 延迟设置

```
module example(input logic a, b, c,  
              output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} = ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;
```

 

# 时序逻辑

- SystemVerilog uses **idioms** (**always**) to describe **latches**, **flip-flops** and **FSMs**

# always 语句

## General Structure:

```
always @(sensitivity list)  
    statement;
```

Whenever the event in sensitivity list occurs,  
statement is executed

# D 触发器 (自己写)


```
module flop(input logic clk,  
            input logic [3:0] d,  
            output logic [3:0] q);
```

```
    always_ff @(posedge clk)
```

```
        q <= d;           // pronounced "q gets (得到) d"
```

```
endmodule
```

## Synthesis:

 

# 可复位的 D 触发器(Flip-Flop) (自己写)


```
module flopr(input logic clk,  
            input logic reset,  
            input logic [3:0] d,  
            output logic [3:0] q);
```

// 同步复位

```
always_ff @(posedge clk)  
    if (reset) q <= 4'b0;  
    else      q <= d;
```

```
endmodule
```

**Synthesis:**

 


# 帶复位 D Flip-Flop

```
module flopr(input logic clk,  
            input logic reset,  
            input logic [3:0] d,  
            output logic [3:0] q);
```

// 异步复位

```
always_ff @(posedge clk, posedge reset)  
    if (reset) q <= 4'b0;  
    else      q <= d;
```

```
endmodule
```

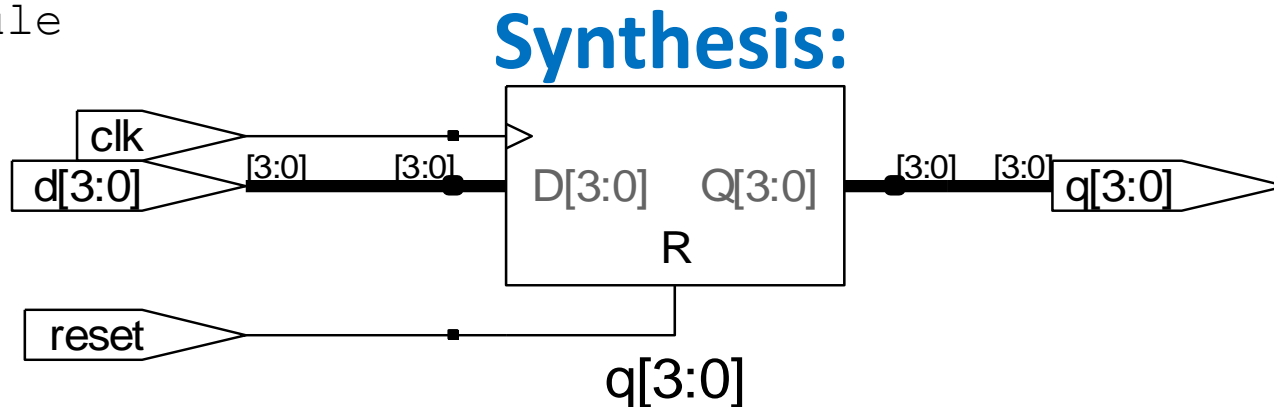

# D Flip-Flop with 使能


```
module flopren(input logic clk,  
              input logic reset,  
              input logic en,  
              input logic [3:0] d,  
              output logic [3:0] q);
```

// 使能与异步复位

```
always_ff @(posedge clk, posedge reset)  
  if (reset) q <= 4'b0;  
  else if (en) q <= d;
```

```
endmodule
```

综合后:

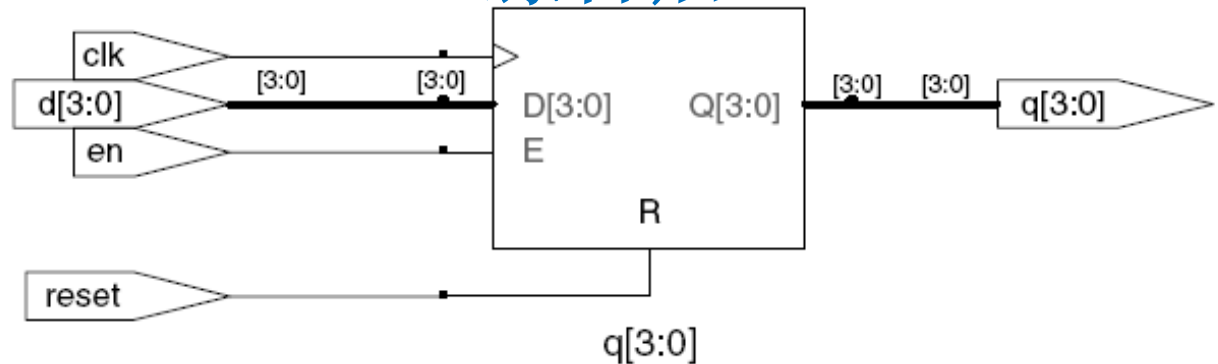




# 锁存器

```
module latch(input logic clk,  
             input logic [3:0] d,  
             output logic [3:0] q);  
  
    always_latch  
        if (clk) q <= d;  
  
endmodule
```

综合后:

 

**Warning:** We don't use latches in this text. But you might write code that inadvertently implies a latch. Check synthesized hardware – if it has latches in it, there's an error.

# 小结

## 通用结构:

```
always @(sensitivity list)  
    statement;
```



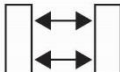
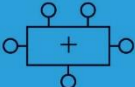

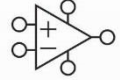

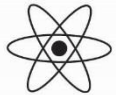
- **Flip-flop:**           always\_ff
- **Latch:**            always\_latch   **(don't use)**

# 其他行为语句 (类似其他编程语言)

- Statements that must be inside `always` statements: (必须在`always`语句内)
  - `if / else`
  - `case, casez`

# 第四章 硬件描述语言

- 介绍
- 组合逻辑
- 结构化模块
- 时序逻辑
- 更多组合逻辑
- 有限状态机
- 参数化模块
- 测试程序

Application Software	<pre>&gt;"hello world!"</pre>
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	



画出HDL代码描述的电路图，简化以便使用最少的门


## SystemVerilog

```
module exercise2(input  logic [3:0] a,  
                 output logic [1:0] y);  
    always_comb  
        if      (a[0]) y = 2'b11;  
        else if (a[1]) y = 2'b10;  
        else if (a[2]) y = 2'b01;  
        else if (a[3]) y = 2'b00;  
        else      y = a[1:0];  
endmodule
```

先画真值表，得到逻辑表达式，再化简。

$$Y_0 = a_0 + a_2 \bar{a}_1 \bar{a}_0 = a_0 + a_2 \bar{a}_1$$
 
$$Y_1 = a_0 + a_1 \bar{a}_0 = a_0 + a_1$$





这两段代码功能一样吗？画出他们的硬件电路图

```
module code1(input logic clk, a, b, c,  
             output logic y);
```

```
  logic x;
```

```
  always_ff @(posedge clk) begin
```

```
    x <= a & b;
```

```
    y <= x | c;
```

```
  end
```

```
endmodule
```

```
module code2 (input logic a, b, c, clk,  
              output logic y);
```

```
  logic x;
```


```
  always_ff @(posedge clk) begin
```

```
    y <= x | c;
```

```
    x <= a & b;
```

```
  end
```

```
endmodule
```

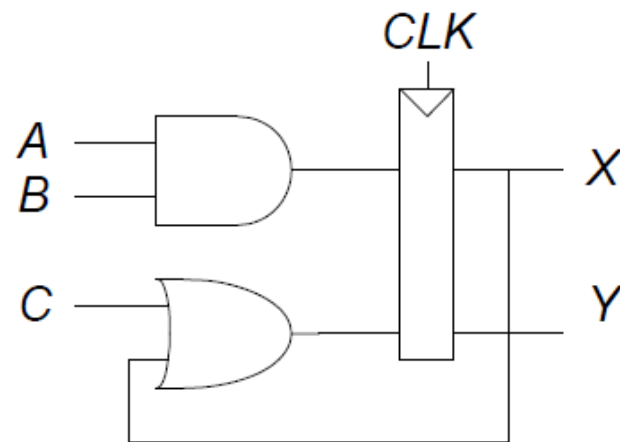

```
module priority(input logic [3:0] a,  
                output logic [3:0] y);  
  
    always_comb  
        if (a[3]) y = 4'b1000;  
        else if (a[2]) y = 4'b0100;  
        else if (a[1]) y = 4'b0010;  
        else if (a[0]) y = 4'b0001;  
endmodule
```

```
    always_comb  
        if (a[3]) y = 4'b1000;  
        else if (a[2]) y = 4'b0100;  
        else if (a[1]) y = 4'b0010;  
        else if (a[0]) y = 4'b0001;  
        else y = 4'b0000;  
endmodule
```

```
module gates(input logic [3:0] a, b,  
            output logic [3:0] y1, y2, y3, y4, y5)  
    always @(a)  
    begin  
        y1 = a & b;  
        y2 = a | b;  
        y3 = a ^ b;  
        y4 = ~(a & b);  
        y5 = ~(a | b);  
    end  
endmodule
```

```
module gates(input logic [3:0] a, b,  
            output logic [3:0] y1, y2, y3, y4, y5);  
    always_comb  
    begin  
        y1 = a & b;  
        y2 = a | b;  
        y3 = a ^ b;  
        y4 = ~(a & b);  
        y5 = ~(a | b);  
    end  
endmodule
```



# 组合逻辑中使用 always

```
// combinational logic using an always statement
module gates(input logic [3:0] a, b,
             output logic [3:0] y1, y2, y3, y4, y5);
    always_comb // need begin/end because there is
    begin      // more than one statement in always
        y1 = a & b; // AND
        y2 = a | b; // OR
        y3 = a ^ b; // XOR
        y4 = ~(a & b); // NAND
        y5 = ~(a | b); // NOR
    end
endmodule
```

This hardware could be described with assign statements using fewer lines of code, so it's better to use assign statements in this case.

# 组合逻辑中使用case

```
module sevenseg(input  logic [3:0] data,
                output logic [6:0] segments);

    always_comb
        case (data)
            //                abc_defg
            0: segments =    7'b111_1110;
            1: segments =    7'b011_0000;
            2: segments =    7'b110_1101;
            3: segments =    7'b111_1001;
            4: segments =    7'b011_0011;
            5: segments =    7'b101_1011;
            6: segments =    7'b101_1111;
            7: segments =    7'b111_0000;
            8: segments =    7'b111_1111;
            9: segments =    7'b111_0011;
            default: segments = 7'b000_0000; // required
        endcase
    endmodule
```


# 组合逻辑中使用case

- case statement implies combinational logic **only if** all possible input combinations described
- Remember to use **default** statement

# 组合逻辑中使用 casez

```
module priority_casez(input  logic [3:0] a,  
                    output logic [3:0] y);  
  
    always_comb  
        casez (a)  
            4'b1???: y = 4'b1000; // ?=don't care  
            4'b01??: y = 4'b0100;  
            4'b001?: y = 4'b0010;  
            4'b0001: y = 4'b0001;  
            default: y = 4'b0000;  
        endcase  
endmodule
```

## Synthesis:

 


# 阻塞 **blocking** vs. 非阻塞赋值 **nonblocking**

- `<=` is **nonblocking** assignment
  - Occurs simultaneously with others (并行)
- `=` is **blocking** assignment
  - Occurs in order it appears in file (串行)


```
// Good synchronizer using  
// nonblocking assignments  
module syncgood(input logic clk,  
                input logic d,  
                output logic q);
```
 
```
    logic n1;  
    always_ff @(posedge clk)  
        begin  
            n1 <= d; // nonblocking  
            q <= n1; // nonblocking  
        end  
endmodule
```



```
// Bad synchronizer using  
// blocking assignments  
module syncbad(input logic clk,  
               input logic d,  
               output logic q);
```
 
```
    logic n1;  
    always_ff @(posedge clk)  
        begin  
            n1 = d; // blocking  
            q = n1; // blocking  
        end  
endmodule
```



# 信号赋值规则

- **Synchronous sequential logic:** use `always_ff @ (posedge clk)` and nonblocking assignments (`<=`)

```
always_ff @(posedge clk)
    q <= d; // nonblocking
```

- **Simple combinational logic:** use continuous assignments (`assign...`)


```
assign y = a & b;
```

- **More complicated combinational logic:** use `always_comb` and blocking assignments (`=`)
- Assign a signal in **only one** `always` statement or continuous assignment statement.

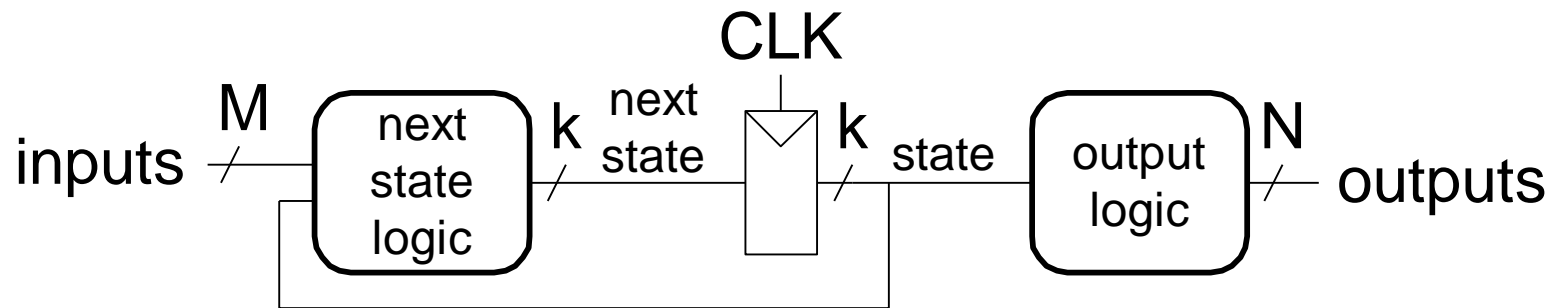
# 有限状态机 (FSMs)

- 三大模块:

- next state logic
- state register
- output logic



# FSM Example: Divide by 3

 

The double circle indicates the reset state



# FSM in SystemVerilog


```
module divideby3FSM(input  logic clk,
                   input  logic reset,
                   output logic q);

    typedef enum logic [1:0] {S0, S1, S2} statetype;
    statetype state, nextstate;


    // state register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else      state <= nextstate;

    // next state logic
    always_comb
        case (state)
            S0:    nextstate = S1;
            S1:    nextstate = S2;
            S2:    nextstate = S0;
            default: nextstate = S0;
        endcase

     // output logic
    assign q = (state == S0);
endmodule
```




# 带输入的FSM

 

看FSM状态图，写出Systemverilog代码
 
# 带输入的FSM

```
module fsmWithInputs(input  logic clk,  
                    input  logic reset,  
                    input  logic a,  
                    output logic q);  
  
typedef enum logic [1:0] {S0, S1, S2} statetype;  
statetype state, nextstate;  
  
// state register  
always_ff @(posedge clk, posedge reset)  
    if (reset) state <= S0;  
    else      state <= nextstate;  
  
// next state logic  
always_comb  
    case (state)  
        S0:      if (a) nextstate = S1;  
                else  nextstate = S0;  
        S1:      nextstate = S2;  
        S2:      if (a) nextstate = S2;  
                else  nextstate = S0;  
        default: nextstate = S0;  
    endcase  
  
// output logic  
assign q = (state == S2);  
endmodule
```



看FSM状态图，写出Systemverilog代码

# 按照HDL代码画出FSM1



## SystemVerilog

```
module fsm2(input logic clk, reset,
            input logic a, b,
            output logic y);


    logic [1:0] state, nextstate;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;
    parameter S3 = 2'b11;

    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;

    always_comb
        case (state)
            S0: if (a ^ b) nextstate = S1;
                else nextstate = S0;
            S1: if (a & b) nextstate = S2;
                else nextstate = S0;
            S2: if (a | b) nextstate = S3;
                else nextstate = S0;
            S3: if (a | b) nextstate = S3;
                else nextstate = S0;
        endcase

    assign y = (state == S1) | (state == S2);
endmodule
```

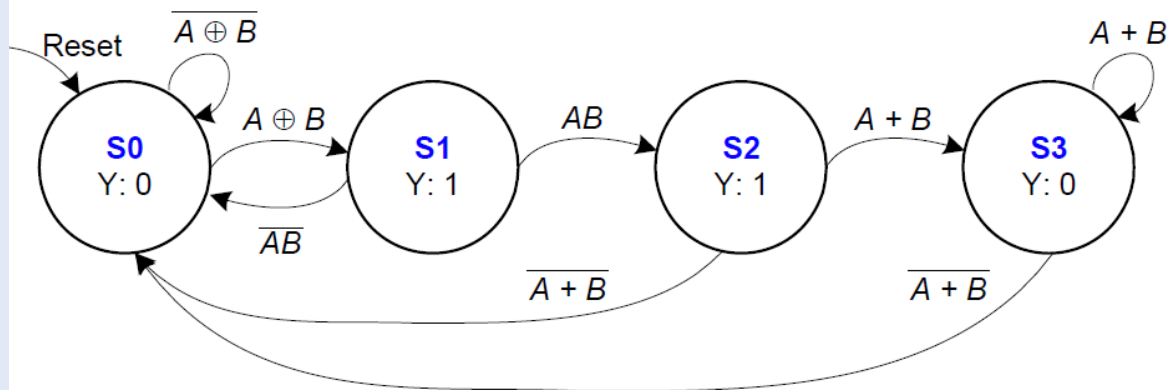

# 出FSM2



```
module fsm1(input logic clk, reset,  
            input logic taken, back,  
            output logic predicttaken);
```

```
logic [4:0] state, nextstate;
```

```
parameter S0 = 5'b00001;
```

```
parameter S1 = 5'b00010;
```

```
parameter S2 = 5'b00100;
```

```
parameter S3 = 5'b01000;
```

```
parameter S4 = 5'b10000;
```

```
always_ff @(posedge clk, posedge reset)
```

```
    if (reset) state <= S2;
```

```
    else      state <= nextstate;
```

```
always_comb
```

```
    case (state)
```

```
        S0: if (taken) nextstate = S1;
```

```
            else      nextstate = S0;
```

```
        S1: if (taken) nextstate = S2;
```

```
            else      nextstate = S0;
```

```
        S2: if (taken) nextstate = S3;
```

```
            else      nextstate = S1;
```

```
        S3: if (taken) nextstate = S4;
```

```
            else      nextstate = S2;
```

```
        S4: if (taken) nextstate = S4;
```

```
            else      nextstate = S3;
```

```
        default:      nextstate = S2;
```

```
    endcase
```

```
assign predicttaken = (state == S4) |
```

```
                      (state == S3) |
```

```
                      (state == S2 && back);
```

```
endmodule
```

systemverilog代码，画出FSM状态图



# 按照HDL代码画出FSM2



```
module fsm1(input logic clk, reset,
            input logic taken, back,
            output logic predicttaken);

logic [4:0] state, nextstate;


parameter S0 = 5'b00001;
parameter S1 = 5'b00010;
parameter S2 = 5'b00100;
parameter S3 = 5'b01000;
parameter S4 = 5'b10000;

always_ff @(posedge clk, posedge reset)
    if (reset) state <= S2;
    else      state <= nextstate;

always_comb
    case (state)
        S0: if (taken) nextstate=S1;
            else      nextstate=S0;
        S1: if (taken) nextstate=S2;
            else      nextstate=S0;
        S2: if (taken) nextstate=S3;
            else      nextstate=S1;
        S3: if (taken) nextstate=S4;
            else      nextstate=S2;
        S4: if (taken) nextstate=S4;
            else      nextstate=S3;
        default:      nextstate=S2;
    endcase

    assign predicttaken = (state == S4) |
        (state == S3) |
        (state == S2 && back);

endmodule
```

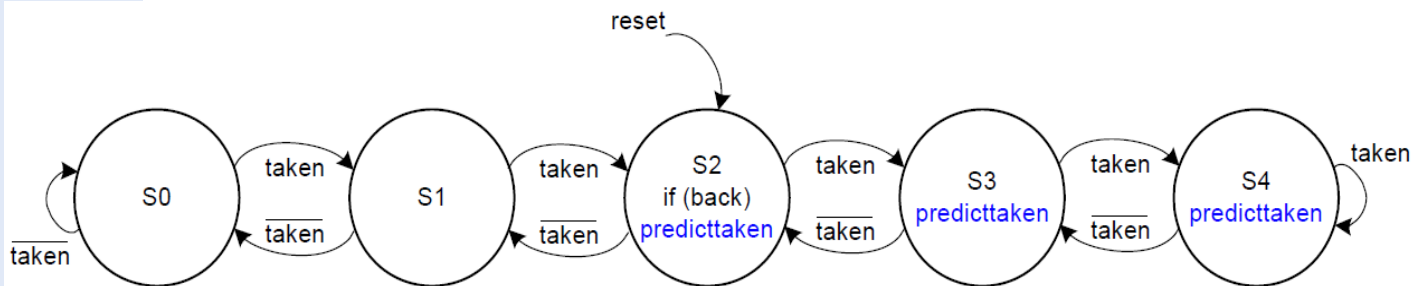

# 参数化模块

## 2:1 mux:

```
module mux2
    #(parameter width = 8) // name and default value
    (input logic [width-1:0] d0, d1,
     input logic s,
     output logic [width-1:0] y);
    assign y = s ? d1 : d0;
endmodule
```

## Instance with 8-bit bus width (uses default):

```
mux2 myMux(d0, d1, s, out);
```

## Instance with 12-bit bus width:

```
mux2 #(12) lowmux(d0, d1, s, out);
```

# 测试程序

- HDL that tests another module: *device under test* (dut)
- 不能综合 **Not synthesizable**
- Uses different features of SystemVerilog
- Types:
  - Simple
  - Self-checking
  - Self-checking with testvectors



# 测试程序例子

- Write SystemVerilog code to implement the following function in hardware:

$$y = \overline{b}c + a\overline{b}$$

- Name the module `sillyfunction`

# Testbench Example

- Write SystemVerilog code to implement the following function in hardware:

$$y = \overline{bc} + a\overline{b}$$

```
module sillyfunction(input  logic a, b, c,
                    output logic y);
    assign y = ~b & ~c | a & ~b;
endmodule
```

# 简单的 Testbench

```
module testbench1();  
    logic a, b, c;  
    logic y;  
    // instantiate device under test  
    sillyfunction dut(a, b, c, y);  
    // apply inputs one at a time  
    initial begin  
        a = 0; b = 0; c = 0; #10;  
        c = 1; #10;  
        b = 1; c = 0; #10;  
        c = 1; #10;  
        a = 1; b = 0; c = 0; #10;  
        c = 1; #10;  
        b = 1; c = 0; #10;  
        c = 1; #10;  
    end  
endmodule
```

# 帶自檢查的 Testbench


```
module testbench2();
    logic a, b, c;
    logic y;
    sillyfunction dut(a, b, c, y); // instantiate dut
    initial begin // apply inputs, check results one at a time
        a = 0; b = 0; c = 0; #10;
        if (y !== 1) $display("000 failed.");
        c = 1; #10;
        if (y !== 0) $display("001 failed.");
        b = 1; c = 0; #10;
        if (y !== 0) $display("010 failed.");
        c = 1; #10;
        if (y !== 0) $display("011 failed.");
        a = 1; b = 0; c = 0; #10;
        if (y !== 1) $display("100 failed.");
        c = 1; #10;
        if (y !== 1) $display("101 failed.");
        b = 1; c = 0; #10;
        if (y !== 0) $display("110 failed.");
        c = 1; #10;
        if (y !== 0) $display("111 failed.");
    end
endmodule
```

# Testbench with 测试向量

- Testvector file: inputs and expected outputs
- Testbench:
  1. Generate clock for assigning inputs, reading outputs
  2. Read testvectors file into array
  3. Assign inputs, expected outputs
  4. Compare outputs with expected outputs and report errors
 
# Testbench with 测试向量

- Testbench clock:
  - assign inputs (on rising edge)
  - compare outputs with expected outputs (on falling edge).



- Testbench clock also used as clock for **synchronous sequential circuits**

# Testvectors 文件

- **File:** `example.tv`
- contains vectors of **abc\_yexpected**

```
000_1
001_0
010_0
011_0
100_1
101_1
110_0
111_0
```

# 1. 产生 Clock

```
module testbench3();
    logic          clk, reset;
    logic          a, b, c, yexpected;
    logic          y;
    logic [31:0]   vectornum, errors;    // bookkeeping variables
    logic [3:0]    testvectors[10000:0]; // array of testvectors

    // instantiate device under test
    sillyfunction dut(a, b, c, y);

    // generate clock
    always        // no sensitivity list, so it always executes
    begin
        clk = 1; #5; clk = 0; #5;
    end
end
```



## 2. Read Testvectors into Array

```
// at start of test, load vectors and pulse reset
```

```
initial
```

```
begin
```

```
    $readmemb("example.tv", testvectors);
```

```
    vectornum = 0; errors = 0;
```

```
    reset = 1; #27; reset = 0;
```

```
end
```

```
// Note: $readmemb reads testvector files written in
```

```
// hexadecimal
```

# 3. Assign Inputs & Expected Outputs

```
// apply test vectors on rising edge of clk
always @(posedge clk)
  begin
    #1; {a, b, c, yexpected} = testvectors[vectornum];
  end
```

# 4. Compare with Expected Outputs

```
// check results on falling edge of clk
always @(negedge clk)
  if (~reset) begin // skip during reset
    if (y !== yexpected) begin
      $display("Error: inputs = %b", {a, b, c});
      $display("  outputs = %b (%b expected)", y, yexpected);
      errors = errors + 1;
    end
  end

// Note: to print in hexadecimal, use %h. For example,
//          $display("Error: inputs = %h", {a, b, c});
```

# 4. Compare with Expected Outputs

```
// increment array index and read next testvector
    vectornum = vectornum + 1;
    if (testvectors[vectornum] === 4'bx) begin
        $display("%d tests completed with %d errors",
            vectornum, errors);
        $stop;
    end
end
endmodule
```

```
// === and !== can compare values that are 1, 0, x, or z.
```





# 本章结束

作业： **2.38 3.29**，并编写Systemverilog代码及Testbench。

其它课后题及自己练习编程

# 对创新的理解

 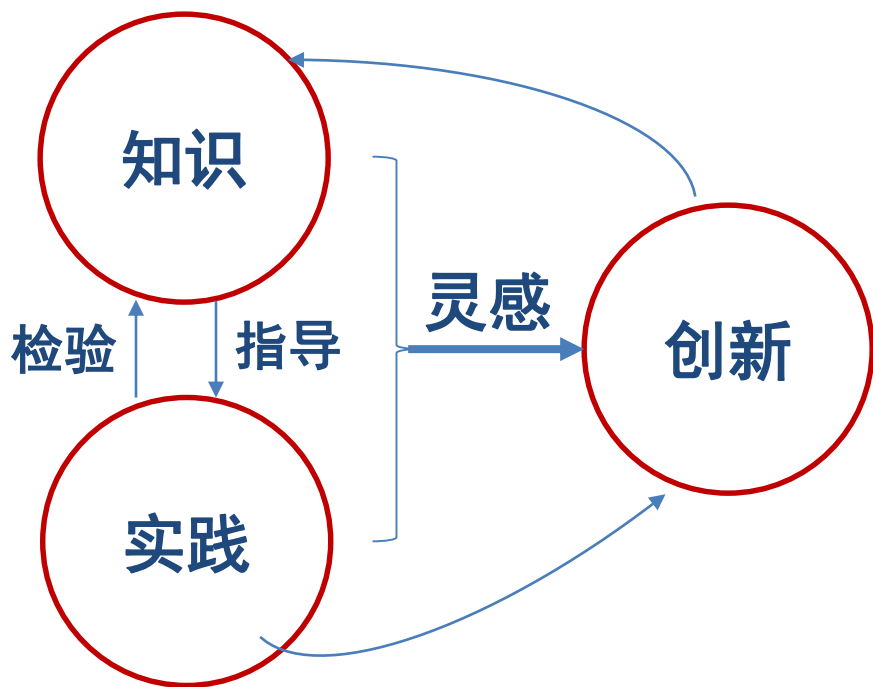


生成式AI将会引起一场机器智能  
新的革命，创业黄金时期

# 实验测试：作业题3.26
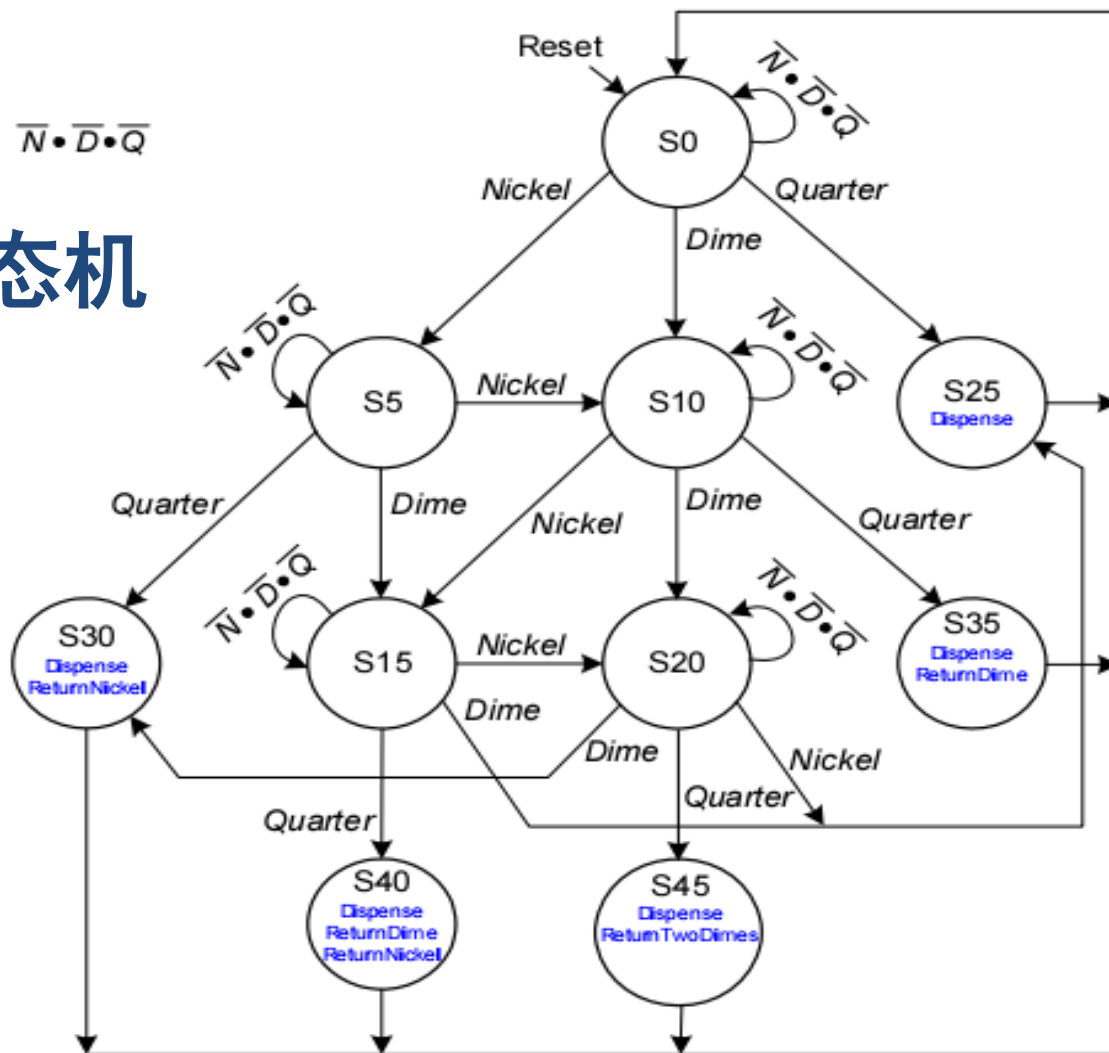
## Moore型状态机

$$\overline{N} \cdot \overline{D} \cdot \overline{Q}$$



Note:  $\overline{N} \cdot \overline{D} \cdot \overline{Q} = \overline{Nickel} \cdot \overline{Dime} \cdot \overline{Quarter}$

# 作业题2.38

$$Y_6 = A_2A_1A_0$$

$$Y_5 = A_2A_1$$


$$Y_4 = A_2A_1 + A_2A_0$$

$$Y_3 = A_2$$

$$Y_2 = A_2 + A_1A_0$$

$$Y_1 = A_2 + A_1$$

$$Y_0 = A_2 + A_1 + A_0$$

 

## SystemVerilog

```
module thermometer(input logic [2:0] a,
                  output logic [6:0] y);

    always_comb
    case (a)
        0: y = 7'b0000000;
        1: y = 7'b0000001;
        2: y = 7'b0000011;
        3: y = 7'b0000111;
        4: y = 7'b0001111;
        5: y = 7'b0011111;
        6: y = 7'b0111111;
        7: y = 7'b1111111;
    endcase
endmodule
```



# 作业题3.29


 


FIGURE 3.8 Waveform showing Z output for Exercise 3.29

# 作业题3.29

设状态表示为  $\{A_{n-1}\}$ ，四个状态  $S_0=0$ ， $S_1=1$

Mealy型状态机

 

$$Z = (A_n + A_{n-1})B + A_n A_{n-1} \overline{B}$$

$$Z = AB + S_0(A+B)$$

# 作业题3.29

## Moore型状态机

设状态表示为  $\{A_{n-1}, A_n\}$ ，四个状态  $S_0=00$ ， $S_1=01$ ， $S_2=10$ ， $S_3=11$

